

Magnetics 101

Rock River Valley IEEE-EMCS

October 27th, 2011

Orin Laney, Atwood Research

Maxwell's Equations: Differential Form -- MKS Units

$$\nabla \cdot \mathbf{D} = \rho$$

$$\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t}$$


$$\nabla \cdot \mathbf{B} = 0$$

$$\nabla \times \mathbf{H} = \frac{\partial \mathbf{D}}{\partial t} + \mathbf{J}$$

FIELDS

TWO KINDS: Electric
Magnetic

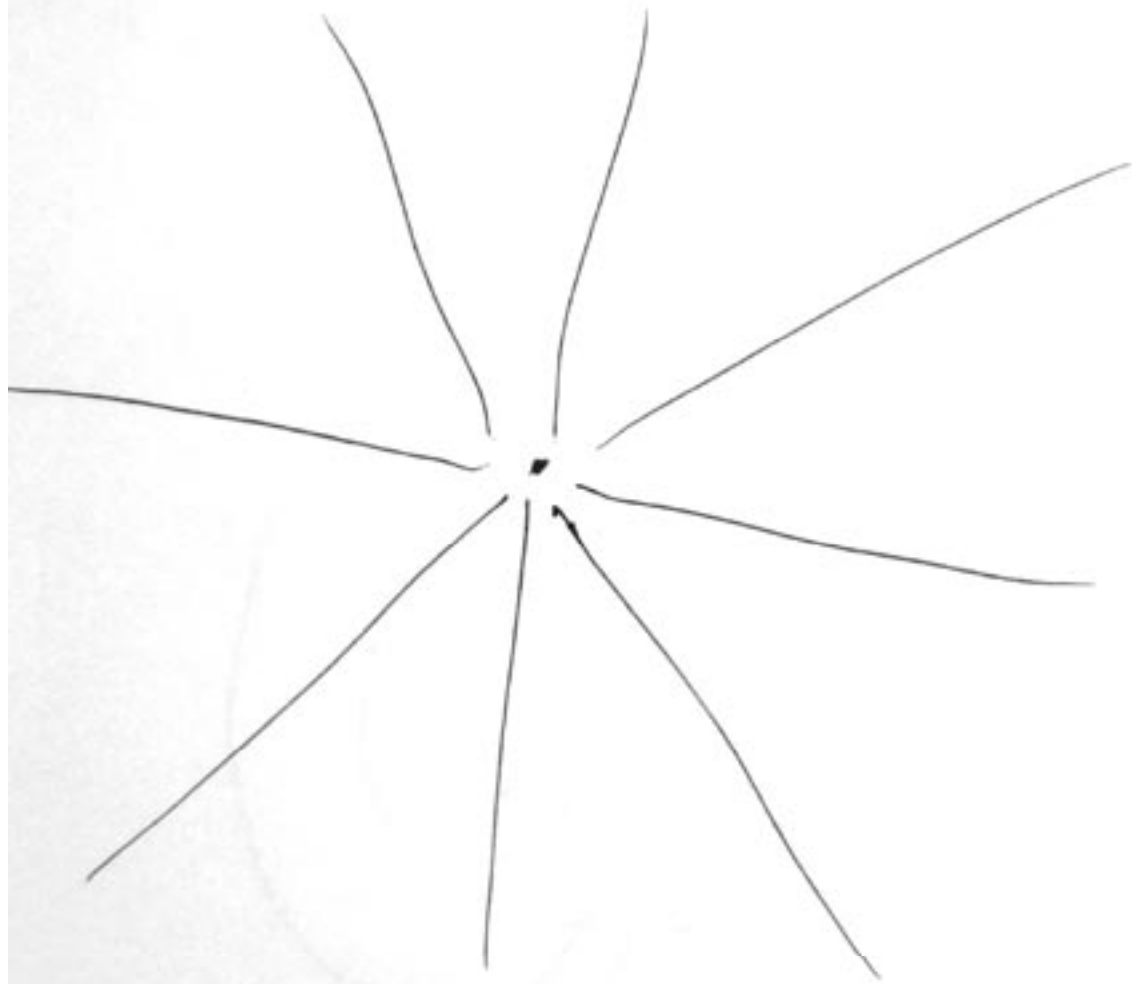
TWO FORMS: Divergent [charge]
Curled [closed loop flux]



Field is conservative
KVL applies

Divergence
has a source
(or sink)

For EM,
it is a
manifestation
of CHARGE

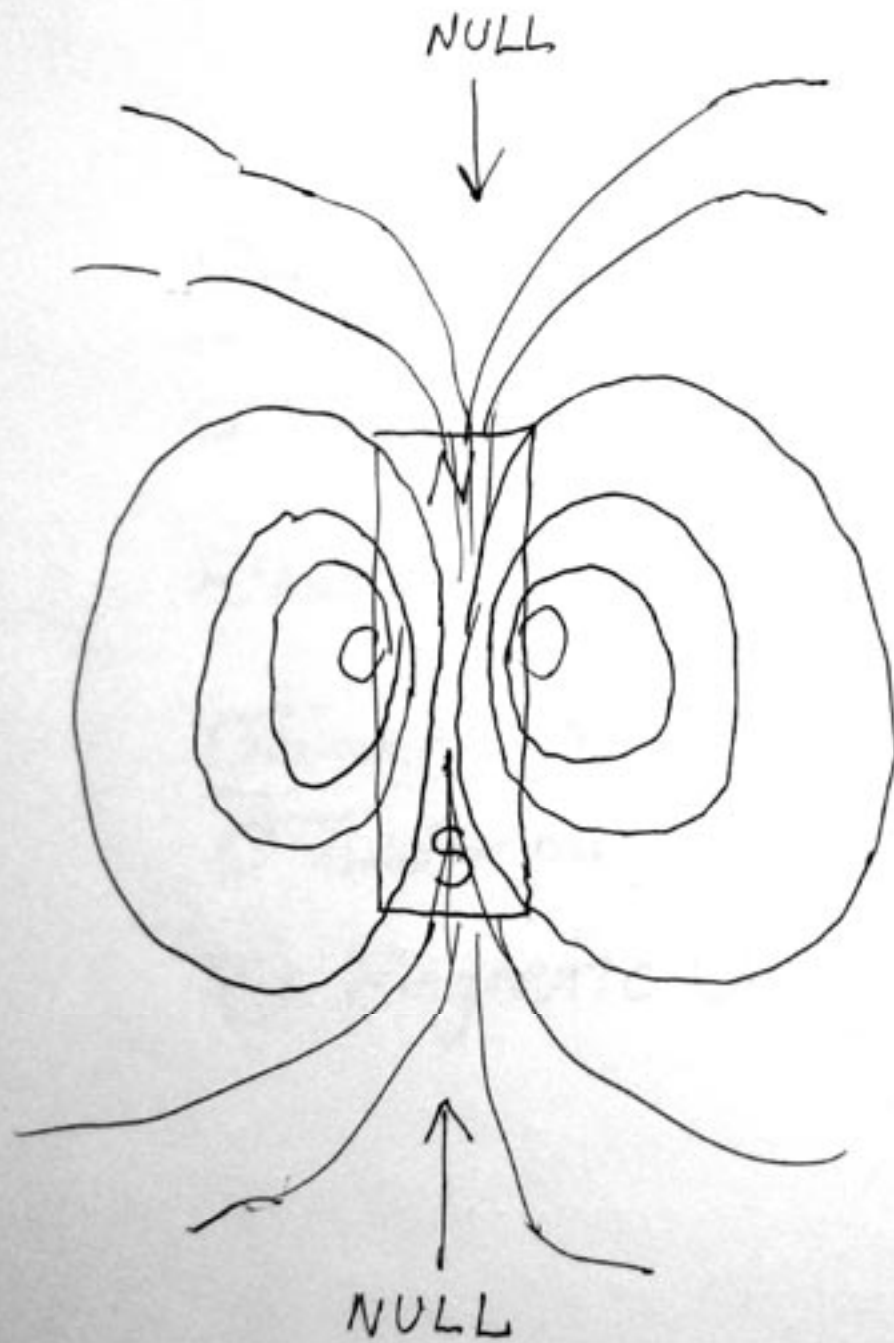

Curl-derived
fields form
closed loops.
No charge is
involved.

FLUX Circuits

Source 1: flow of charge \vec{J}_e (\vec{J}_m)

Source 2: conversion via flux change

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t} \quad \nabla \times \vec{H} = \frac{\partial \vec{D}}{\partial t} + \vec{J}$$

Vacuum has flux conductivities

$$\epsilon_0 \approx 8.854 \times 10^{-12}$$

$$\mu_0 = 4\pi \times 10^{-7}$$

$$c = (\epsilon_0 \mu_0)^{-\frac{1}{2}} \\ = 299792458 \text{ m/s}$$

Bob Golka's Tesla Coil



Playing with magnets

Like poles repel

Opposite poles attract




**AC Levitation: No Connection
but Plenty of Induced Current!**


Pot Core



Laminated Cores

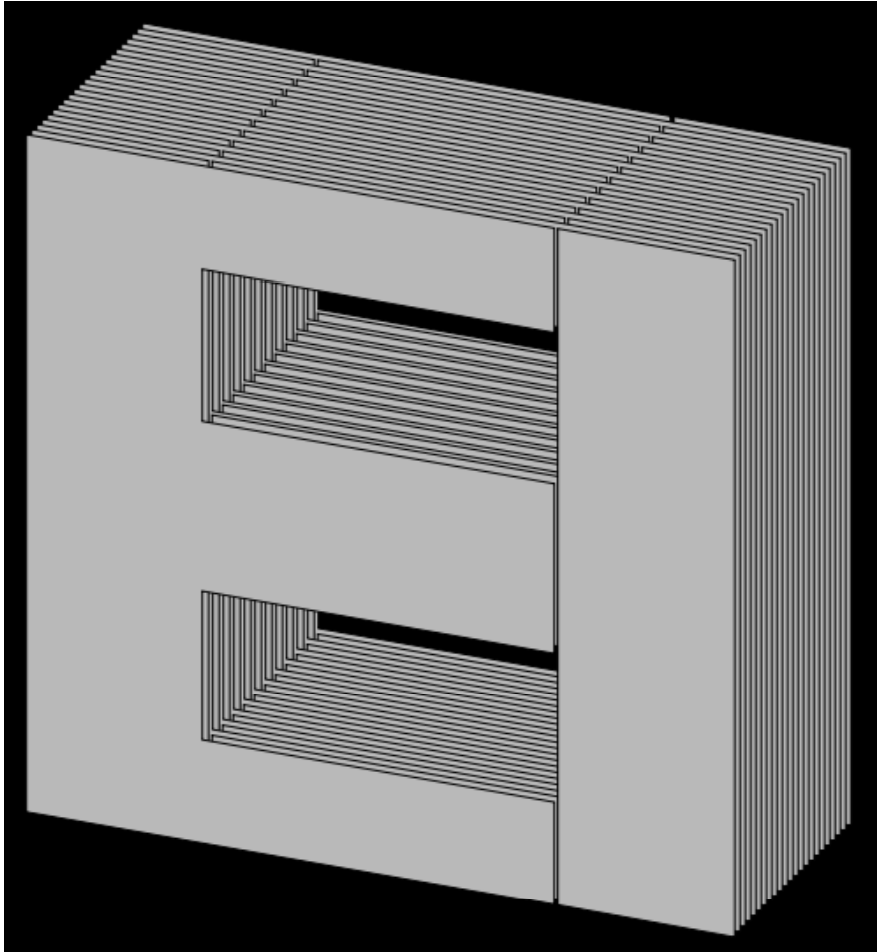

Toroid Winding

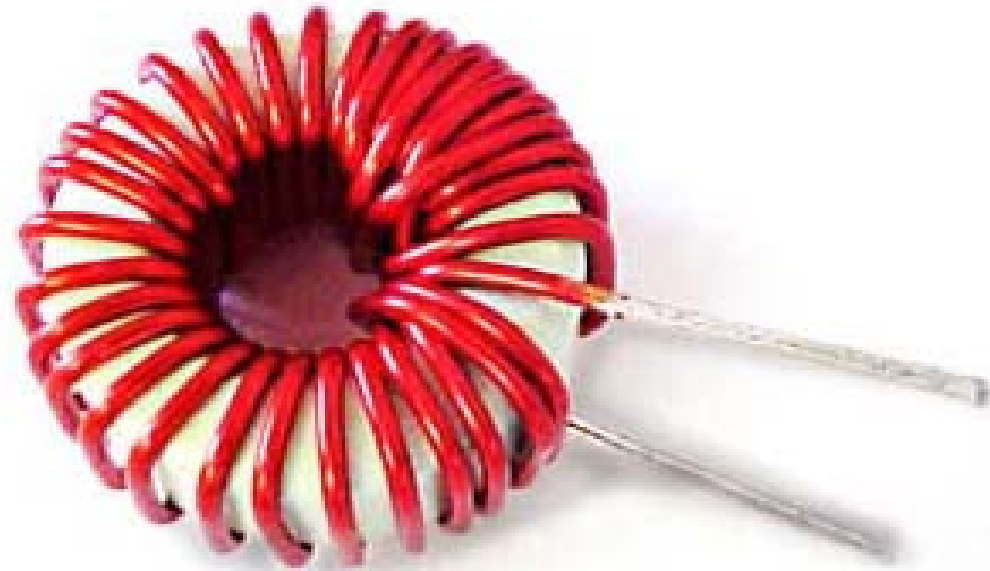


Cut Cores



Inductors

- Inductor self resonance is parallel (high Z)
- Above self resonance, Z is capacitive and lossy
- Single layer coils have highest SRF for a given L
- Minimum Z is DCR
- Q can range from >100 to <5 , has peak

Q Curve Example

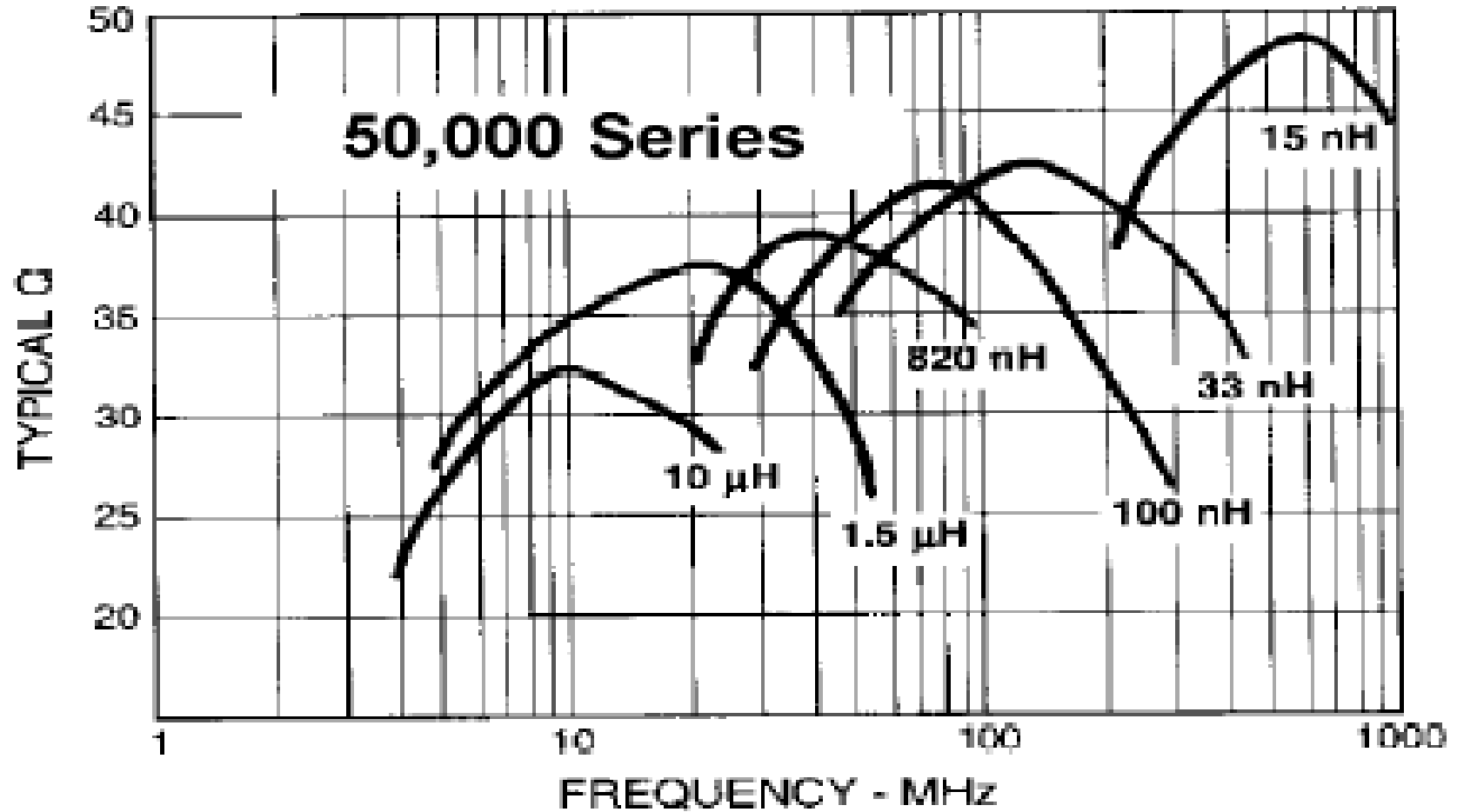


Rod Core Inductor




Transformer Uses


- Voltage Transformer
- Current Transformer
- Isolation Transformer
- Impedance Conversion
- Mode Conversion (Balun)
- Mode Chokes
- Phase & Balance mgmt.

Ideal Transformer

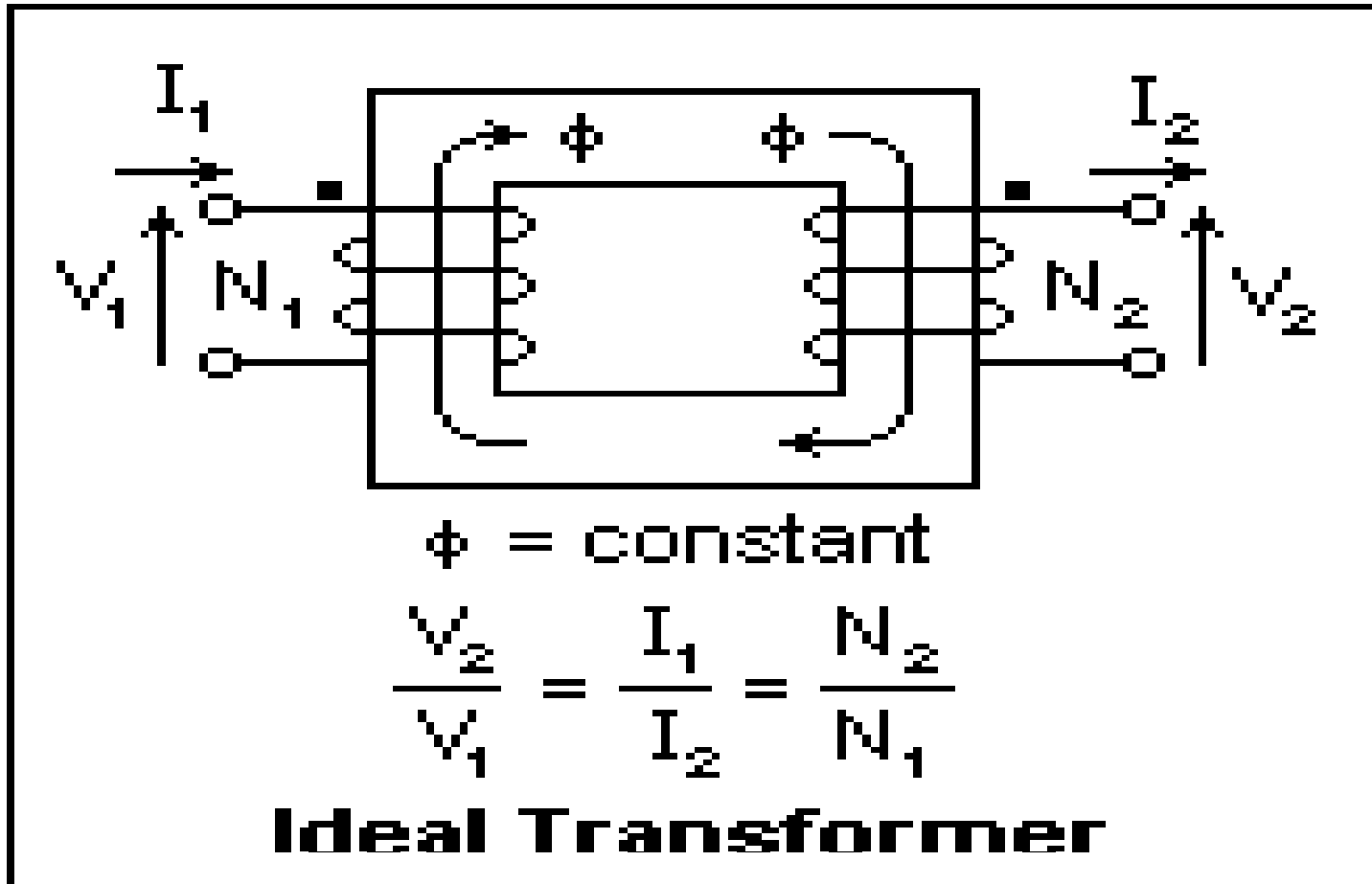


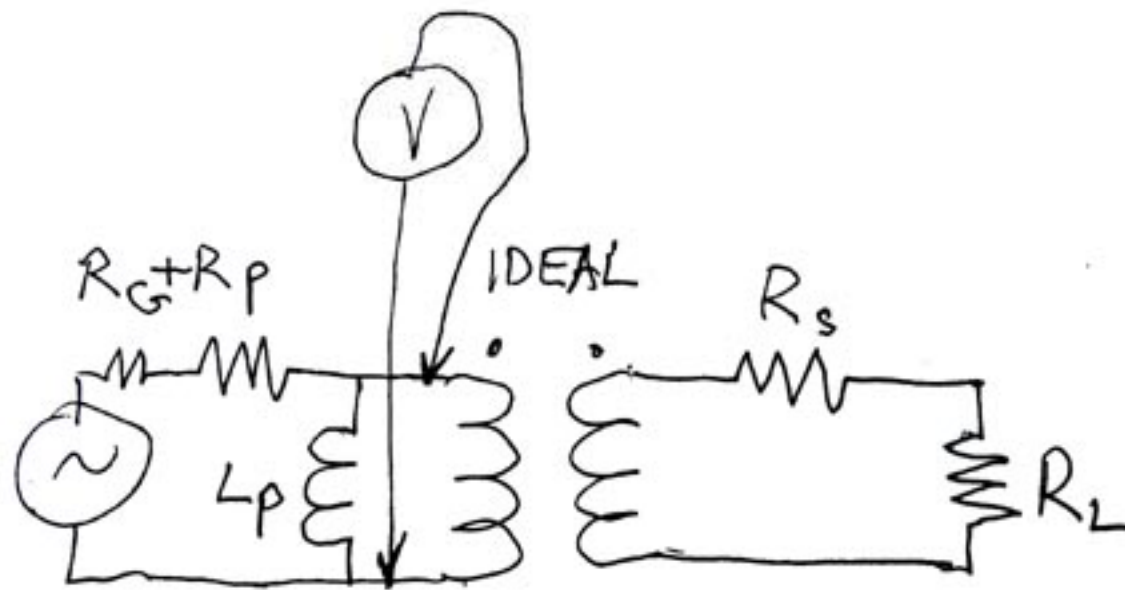


SIMPLIFIED LF MODEL

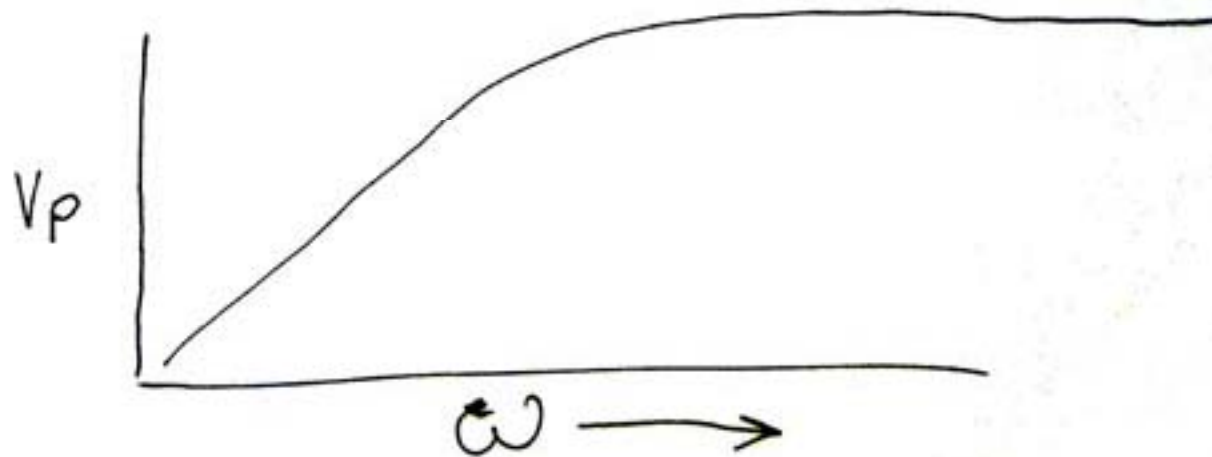


Equivalent Circuit of a Real Xfmr

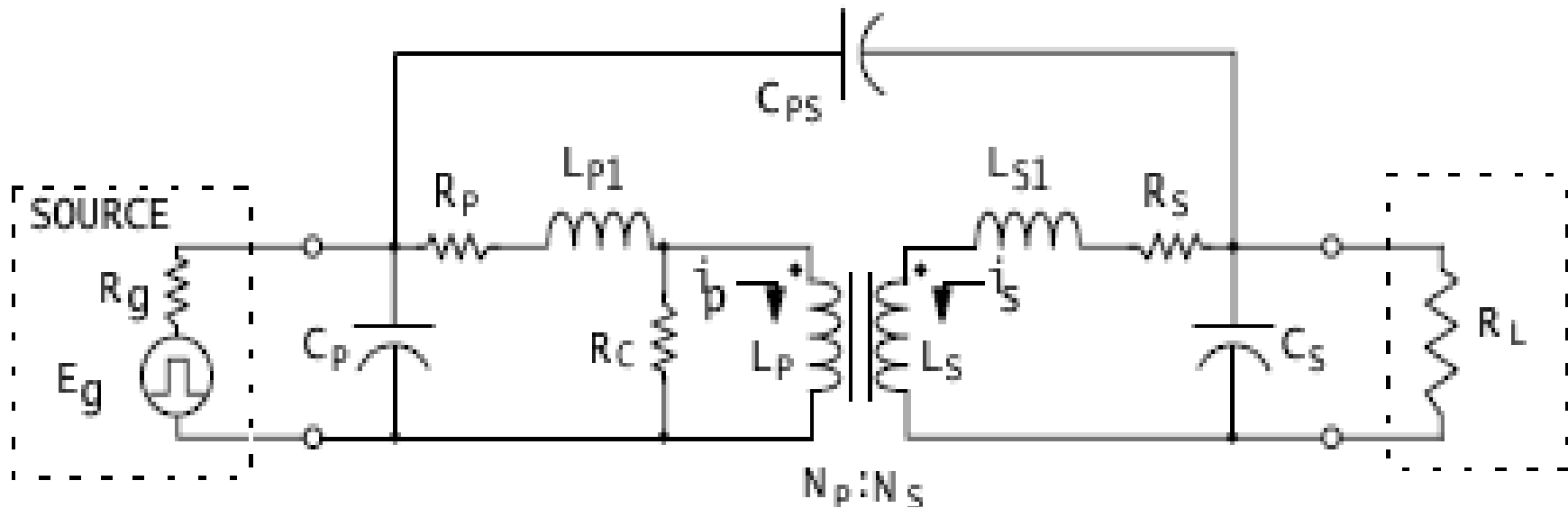


Transformer Frequency Response

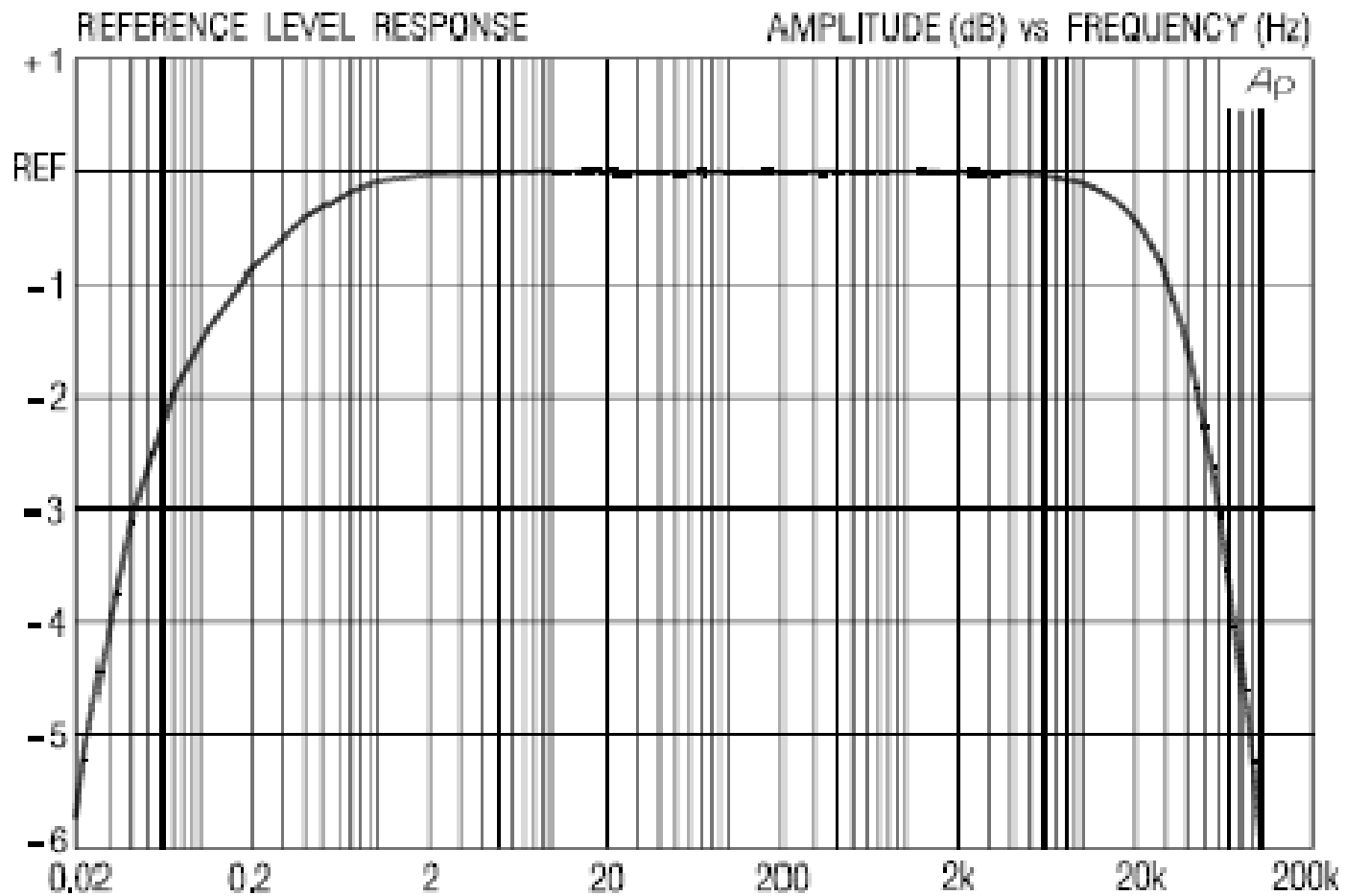


Response as Insertion Loss

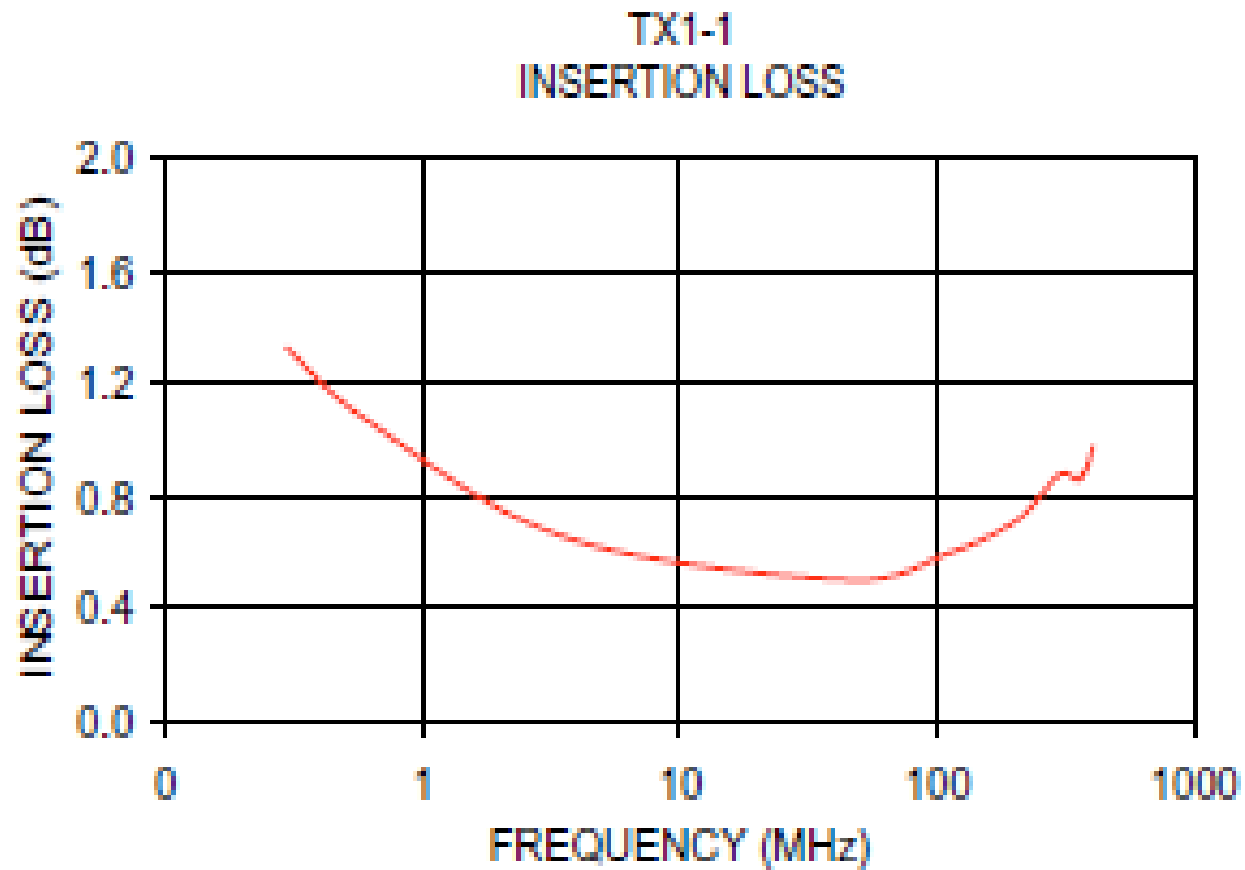


Balanced Model

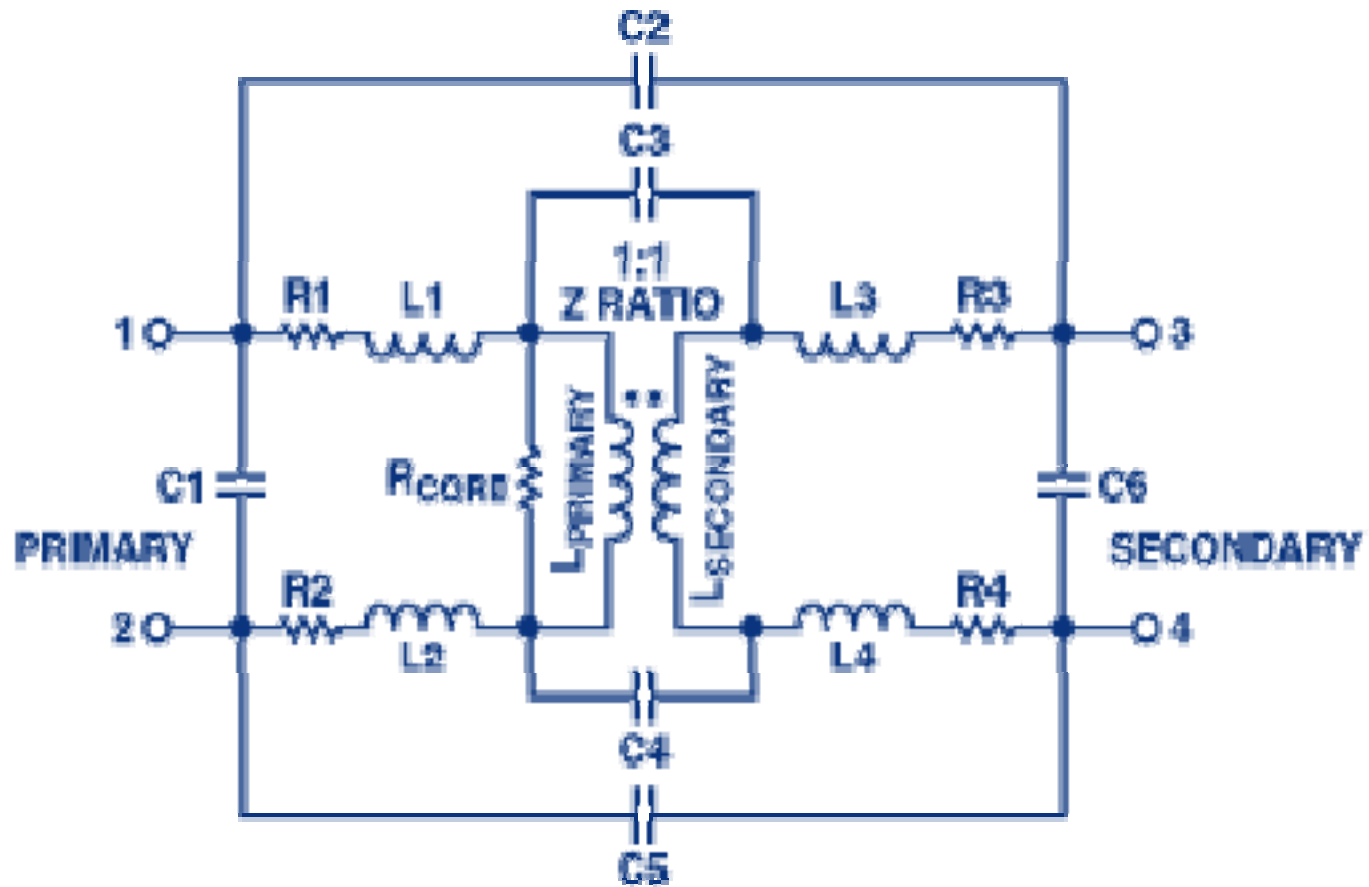


Transformer Stray Capacitance

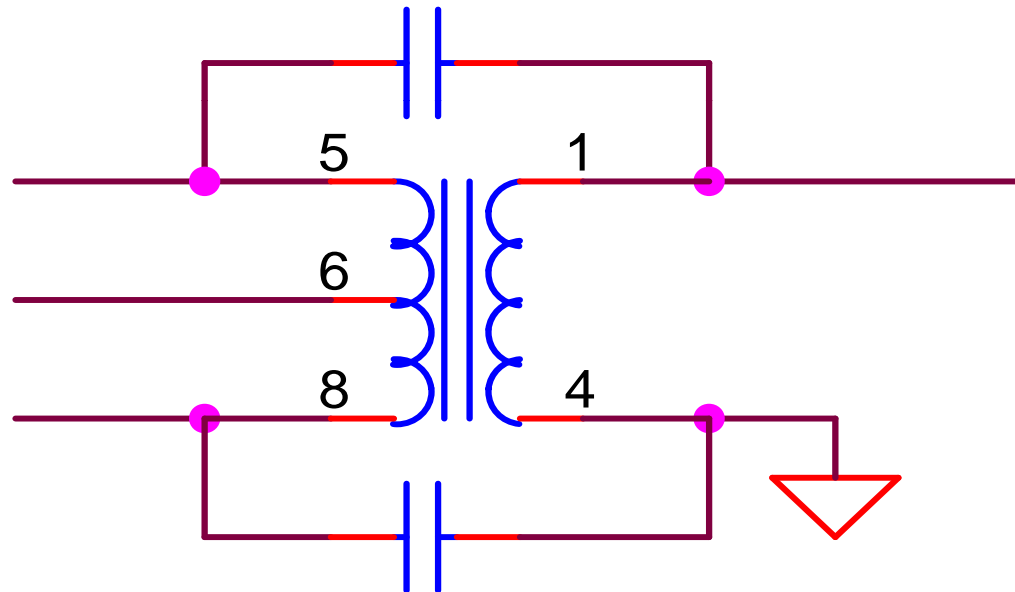


Transformer + CM Choke

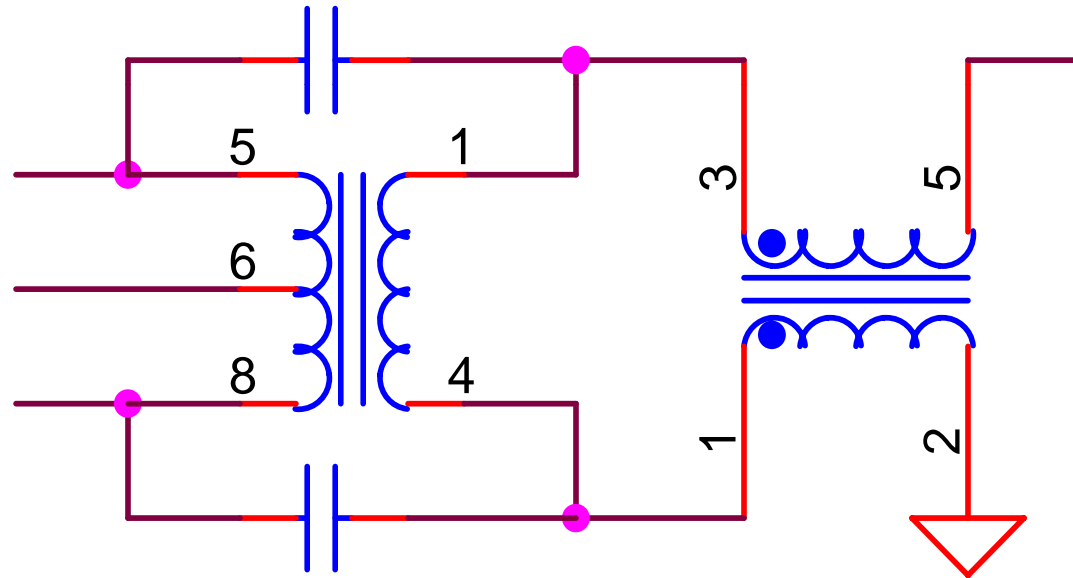


Separating CM & DM

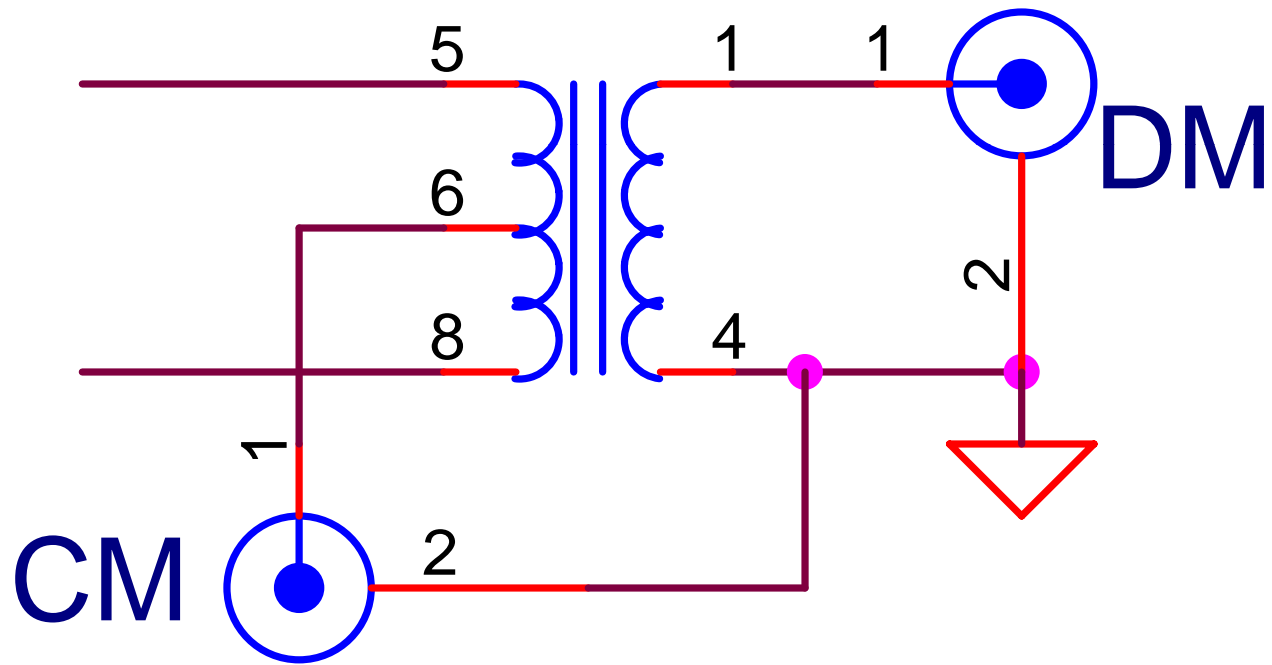


Audio Coupling Xfmr

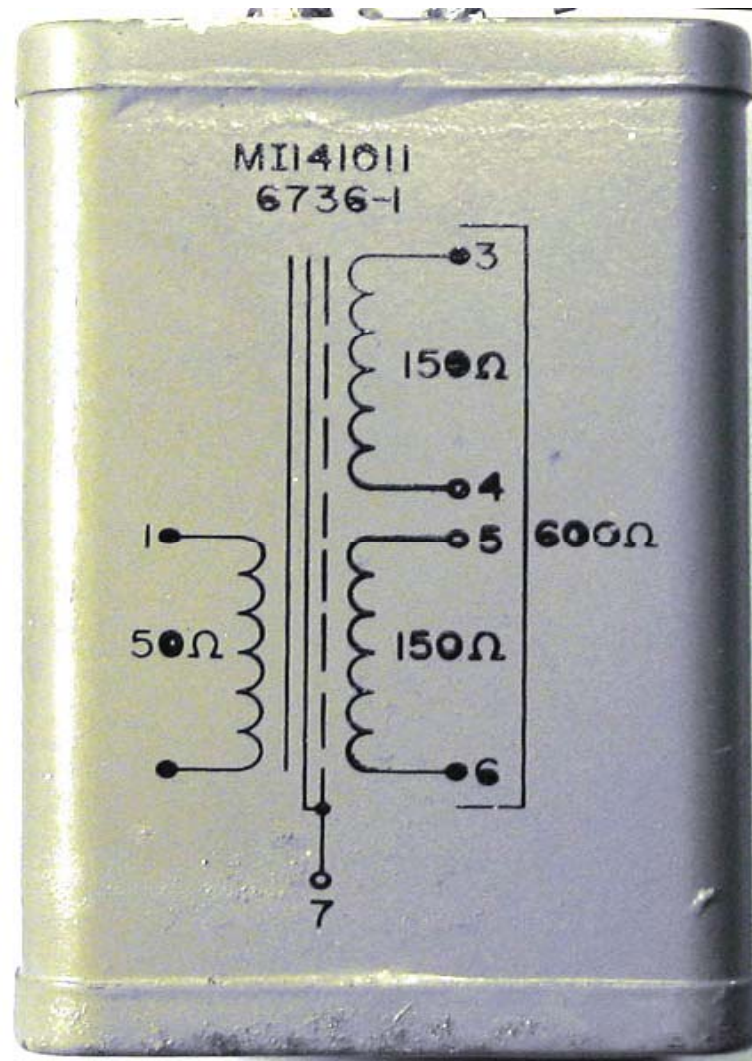


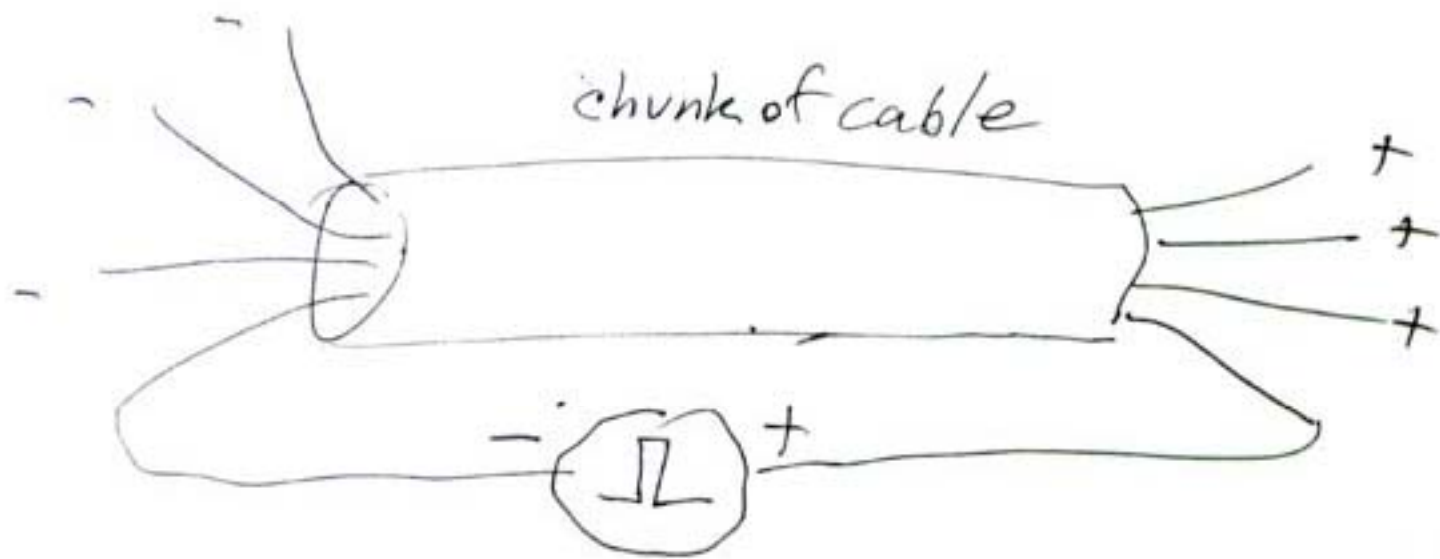


INSTANTANEOUS POLARITY

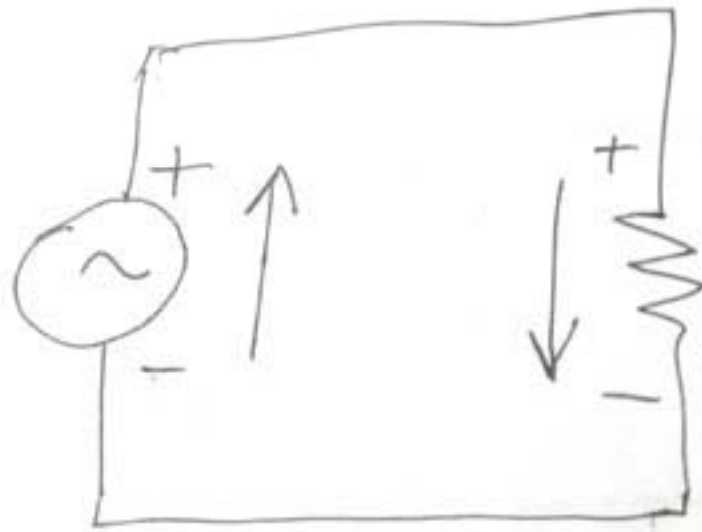

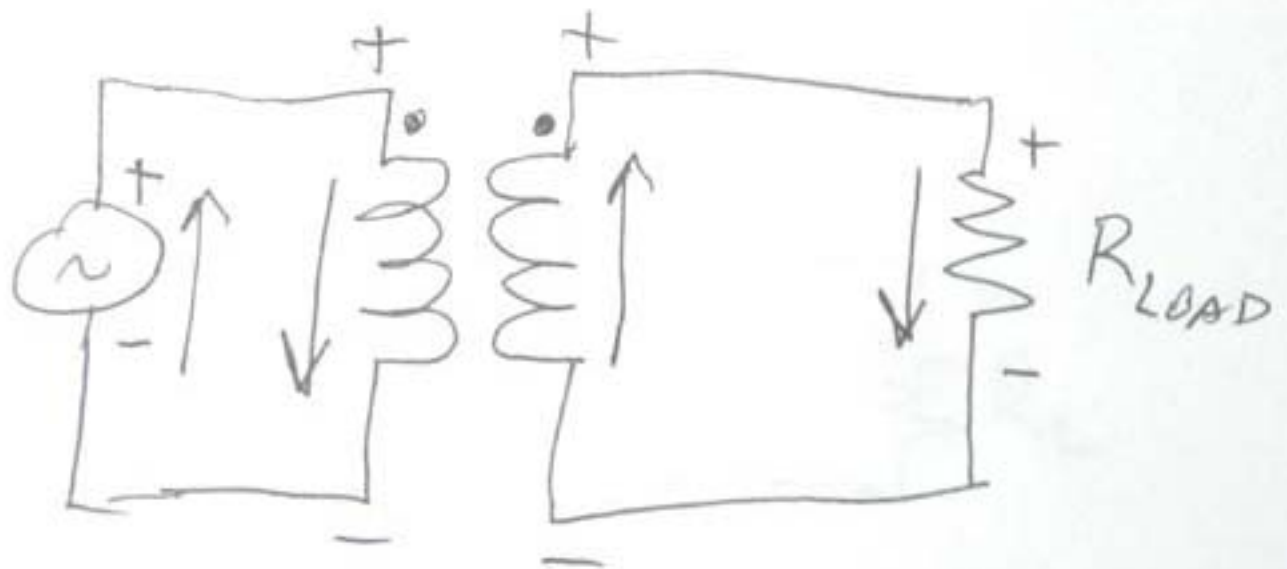
Current Direction Opposite
Between Source and Sink



LF MODEL

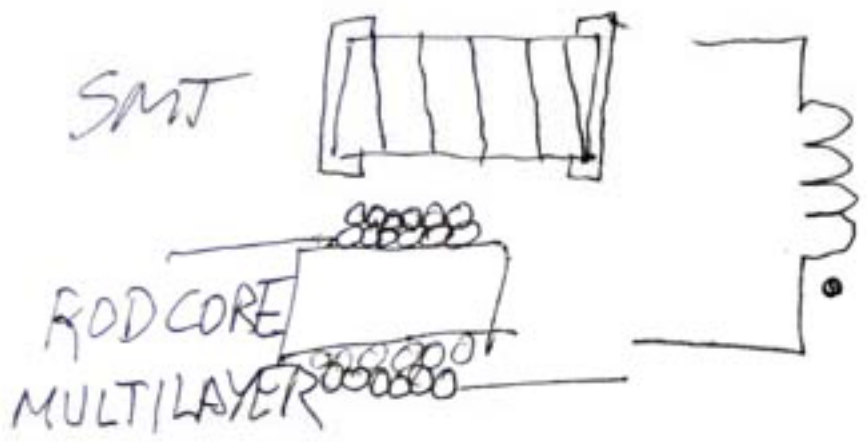

STD

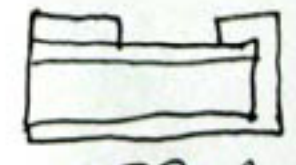


TERM



TUBULAR



MLCC

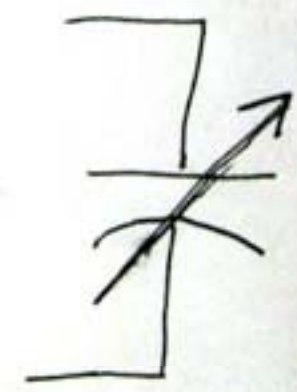

TRIMCAP

Thank You For Coming

www.orinlaney.com